

# Laboratory Manual

**EE-153L – Introduction to Electrical Engineering**

**Fall 2025**


Instructor

**Engr. Noman Khan**

Lab Engineers

**Engr. Bilal Haider**

**Engr. Yasir Kamal**

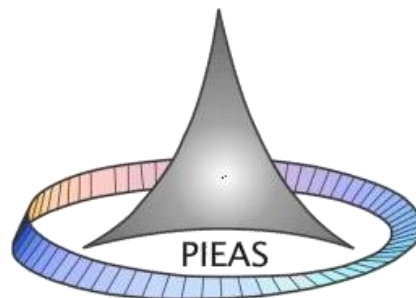

**Department of Electrical Engineering  
Pakistan Institute of Engineering & Applied Sciences  
Islamabad, Pakistan**

## Experiment 8

### Verification of Superposition Theorem

#### 8.1 Objective

The objective of this exercise is to investigate the application of the superposition theorem to multiple DC source circuits in terms of both voltage and current measurements. Moreover, power calculations will also be examined.

#### 8.2 Theory Overview

The superposition theorem states that in a linear bilateral multi-source DC circuit, the current through or voltage across any particular element may be determined by considering the contribution of each source independently, with the remaining sources replaced with their internal resistance. The contributions are then summed, paying attention to polarities, to find the total value. Superposition cannot in general be applied to non-linear circuits or to non-linear functions such as power.

##### 8.2.1 Pre-Lab Task

Before performing the experiment in the laboratory, complete the following tasks in LTspice to demonstrate your understanding of the theoretical concepts. These preparatory tasks will help you predict circuit behavior and verify your results during the lab session.

#### 8.3 Equipment

- Adjustable DC Power Supply
- Digital Multimeter
- 4.7 k $\Omega$ , 6.8 k $\Omega$ , 10 k $\Omega$ , 22 k $\Omega$ , 33 k $\Omega$

#### 8.4 Schematics

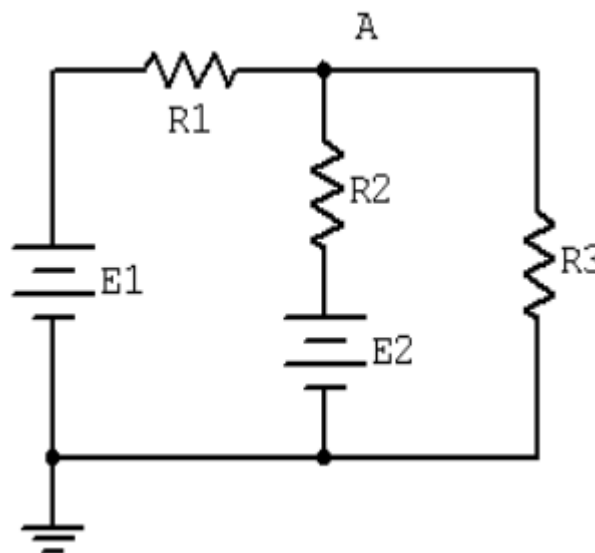


Fig 8.1

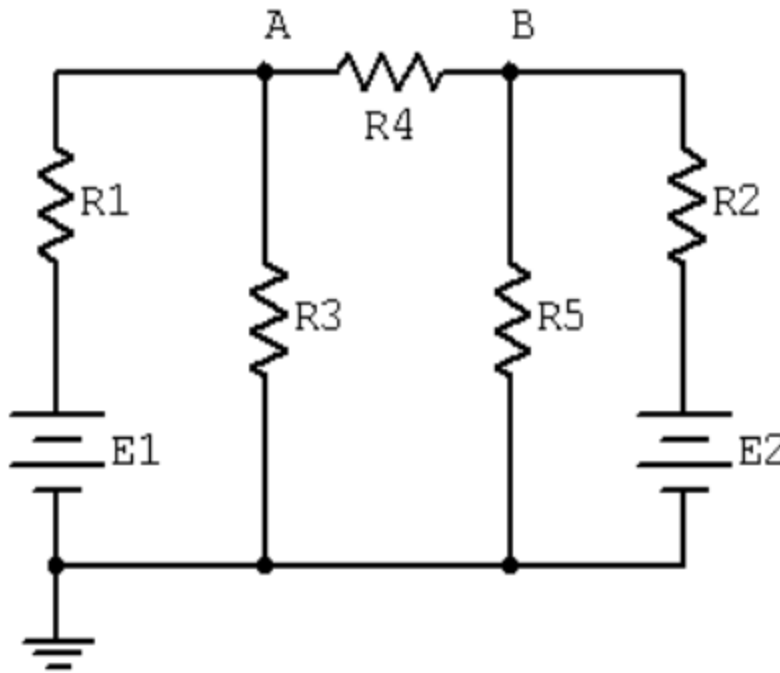


Fig 8.2

## 8.4 Procedure

### Voltage Application

1. Consider the dual supply circuit of Figure 8.1 using  $E1 = 10$  volts,  $E2 = 15$  volts,  $R1 = 4.7$  k,  $R2 = 6.8$  k and  $R3 = 10$  k. To find the voltage from node A to ground, superposition may be used. Each source is considered by itself. First consider source  $E1$  by assuming that  $E2$  is replaced with its internal resistance (a short). Determine the voltage at node A using standard series-parallel techniques and record it in Table 8.1. Make sure to indicate the polarity. Repeat the process using  $E2$  while shorting  $E1$ . Finally, sum these two voltages and record in Table 8.1.
2. To verify the superposition theorem, the process may be implemented directly by measuring the contributions. Build the circuit of Figure 8.1 with the values specified in step 1, however, replace  $E2$  with a short. Do not simply place a shorting wire across source  $E2$ . This will overload the power supply.
3. Measure the voltage at node A and record in Table 8.1. Be sure to note the polarity.
4. Remove the shorting wire and insert source  $E2$ . Also, replace source  $E1$  with a short. Measure the voltage at node A and record in Table 8.1. Be sure to note the polarity.

5. Remove the shorting wire and re-insert source E1. Both sources should now be in the circuit. Measure the voltage at node A and record in Table 8.1. Be sure to note the polarity. Determine and record the deviations between theory and experimental results.

### Current and Power Application

6. Consider the dual supply circuit of Figure 8.2 using  $E1 = 10$  volts,  $E2 = 15$  volts,  $R1 = 4.7$  k,  $R2 = 6.8$  k,  $R3 = 10$  k,  $R4 = 22$  k and  $R5 = 33$  k. To find the current through  $R4$  flowing from node A to B, superposition may be used. Each source is again treated independently with the remaining sources replaced with their internal resistances. Calculate the current through  $R4$  first considering  $E1$  and then considering  $E2$ . Sum these results and record the three values in Table 8.2.
7. Assemble the circuit of Figure 8.2 using the values specified. Replace source  $E2$  with a short and measure the current through  $R4$ . Be sure to note the direction of flow and record the result in Table 8.2.
8. Replace the short with source  $E2$  and swap source  $E1$  with a short. Measure the current through  $R4$ . Be sure to note the direction of flow and record the result in Table 8.2.
9. Remove the shorting wire and re-insert source  $E1$ . Both sources should now be in the circuit. Measure the current through  $R4$  and record in Table 8.2. Be sure to note the direction. Determine and record the deviations between theory and experimental results.
10. Power is not a linear function as it is proportional to the square of either voltage or current. Consequently, superposition should not yield an accurate result when applied directly to power. Based on the measured currents in Table 8.2, calculate the power in  $R4$  using  $E1$ -only and  $E2$ -only and record the values in Table 8.3. Adding these two powers yields the power as predicted by superposition. Determine this value and record it in Table 8.3. The true power in  $R4$  may be determined from the total measured current flowing through it. Using the experimental current measured when both  $E1$  and  $E2$  were active (Table 8.2), determine the power in  $R4$  and record it in Table 8.3.

### 8.6 Data Tables

Source	$V_A$ Theory	$V_A$ Experimental	Deviation
E1 Only			

E2 Only			
E1 and E2			

*Table 8.1*

<b>Source</b>	<b><math>I_{R4}</math> Theory</b>	<b><math>I_{R4}</math> Experimental</b>	<b>Deviation</b>
E1 Only			
E2 Only			
E1 and E2			

*Table 8.2*

<b>Source</b>	<b><math>P_{R4}</math></b>
E1 Only	
E2 Only	
E1 and E2	

*Table 8.3*

## 8.7 Questions

1. Based on the results of Tables 8.1, 8.2 and 8.3, can superposition be applied successfully to voltage, current and power levels in a DC circuit?
2. If one of the sources in Figure 8.1 inserted with the opposite polarity, would there be a significant change in the resulting voltage at node A? Could both the magnitude and polarity change?
3. Why is it important to note the polarities of the measured voltages and currents?

## 8.8 Conclusion

### Assessment

Sr. No.	Specific Course Learning Outcomes	Knowledge Domains	Performance indicator
Upon completion of this course, the students will be able to			
1	<b>USE</b> electronic lab instruments including the digital multi-meter, function generator, oscilloscope and electronic circuit trainer.	P1	<ul style="list-style-type: none"><li>• Proper wiring of the circuit</li><li>• Correct use of instruments (signal generator, oscilloscope)</li><li>• Data recorded in table</li></ul>
2	<b>CONSTRUCT</b> and <b>ANALYZE</b> basic circuits.	P2	<ul style="list-style-type: none"><li>• Relate experiment with theoretical concept discussed in class.</li><li>• Describe relevant mathematical equations</li><li>• Discuss discrepancies between theoretical, simulation and experimental results</li><li>• Possible sources of discrepancies and ways to improve</li></ul>
3	<b>COMMUNICATE</b> clearly and effectively through presentation and/or report	A2	<ul style="list-style-type: none"><li>• Report is structured properly</li><li>• Figures and Graphs annotated</li><li>• Language is clear</li></ul>
4	<b>DEMONSTRATE</b> teamwork and show commitment to the group in achieving the objectives of laboratory	A2	<ul style="list-style-type: none"><li>• Does his/her part in the group</li><li>• Listen to other's ideas</li><li>• Does not argue</li></ul>
5	<b>DEMONSTRATE</b> punctuality, dress appropriately and comply with the standard safety procedures of the lab	A2	<ul style="list-style-type: none"><li>• Wear proper dress to perform the tasks and Follow lab timing</li><li>• Follow safety instructions for handling the instruments.</li></ul>